

Question 1

a) There are 6 errors as follows:

L1 entity demo is remove oo

L2 missing ;

L3 missing ; and vector out1: out stat - logic\_vector ;

L8

L9 missing process before a case statement


Line 19 remove end if

b) This is a finite state machine

There are 4 states: S0, S1, S2, S3

Reset = 1 system starts at S0

 Depending on in1 input the next state is decided upon rising edge of the clock



Q2


a) Three most common logic implementation in FPGAs are

Look up Tables - SRAM and EPROM - 2-1 MUX

the look up table using memory and 2-1 MUX is a convenient way of applying any function. The 2-1 MUX is simple and fast needing 2 Transistors and one inverter. It can implement any logic gates required.

b)

i)

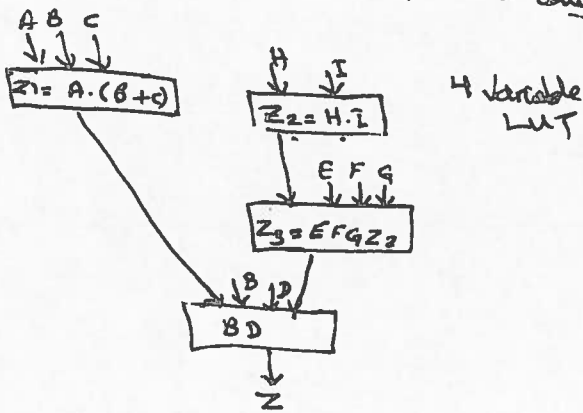

4 variable LUT

Total Area

4 variable LUT requires  $2^4 - 1 = 15$  2-1 MUX

\* Area =  $4 * (2^4 - 1) = 60$  2-1 MUX

Delay


4 variable LUT has 4 2-1 MUX delay

\*  $3 * 4 = 12$  2-1 MUX delay

iii

Using a 3 variable LUT

3 variable LUT

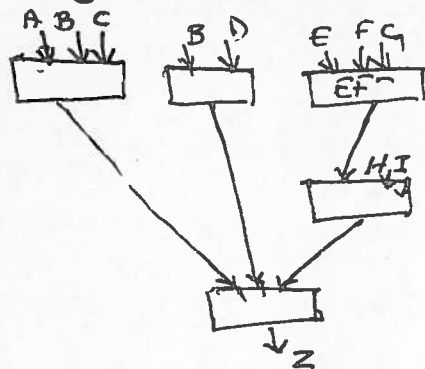


Area =  $5 * (2^3 - 1) = 35$  2-1 MUX delay

Delay =  $3 * 3 = 9$  2-1 MUX delay

ii

A better implementation would be

 

4 variable LUT

Area  $3 * (2^4 - 1) = 45$  MUX delay


Depth  $2 * 4 = 8$  MUX speed

Q 3

a) Advantage of Booth Algorithm is many folds including:  
 applicable to sign & unsigned number multiplication.  
 It reduces the number of rows to be added, hence

b)

20 = 0010100	-20 = 1101100	-40 = 11011000
15 = 0011111	-15 = 1100011	-30 = 11000110

 


-1 → 20

0000	0010100	0000
0000	0011111	0000
1101100		


Result 11011010100 A negative number = 0001001100 =

So the results is 00100101100 = -300

 


b) If we take 15 as the multiplicand then

-20	1101100	adding '0'
00	0000000000	
-15	1111100001	
-15	11100001	

 


 Result → 111011010100 taking the Complement of the number  
 000100101100 = 300



Q4

State Diagram

 

Transition Table

y <sub>1</sub> y <sub>0</sub>	Next States			
	00	01	11	10
00	01	00	01	00
01	10	00	10	00
11	11	11	11	11
10	11	00	11	00

y <sub>1</sub> y <sub>0</sub>	output			
	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	1	1	0


$Z = y_1 y_0 + y_1 \bar{y}_0 (A \oplus B)$  Equ 1

y <sub>1</sub> y <sub>0</sub>	AB			
	00	01	11	10
00	0	0	0	0
01	1	0	1	0
11	1	1	1	1
10	1	0	1	0

$y_1 = y_1 y_0 + (A \oplus B)(y_1 \oplus y_0)$  Equ 2

y <sub>1</sub> y <sub>0</sub>	AB			
	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	1	1	1	1
10	1	0	1	0

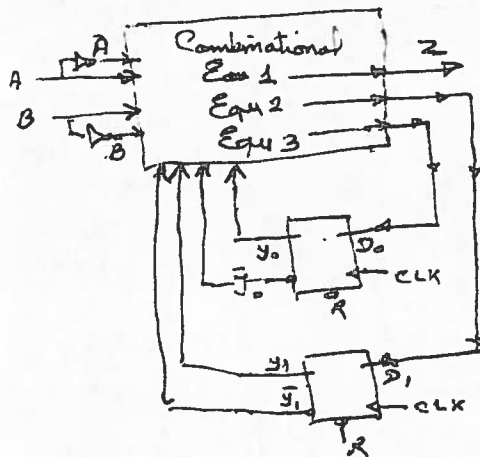$y_0 = y_1 y_0 + (A \oplus B)(y_1 \oplus y_0)$  Equ 3



Q5

Given information

Cycle  $T = 20\text{ ns}$ , clock skew  $\alpha = 2\text{ ns}$ , FF  $t_{cq} = 6\text{ ns}$   
 $t_{su} = 4\text{ ns}$   
 $t_h = 2\text{ ns}$

gate delays  
 NAND  $0.2\text{ ns}$   
 Invert  $0.15\text{ ns}$   
 XOR  $0.3\text{ ns}$   
 MUX  $0.4\text{ ns}$

d)

Node	Arrival time (ns)	Required Time (ns)	Slack (ns)
a	6		
b	6	17.3	11.3
c	6	17.1	11.1
d	6.65	16.95	10.95
e	6.65	17.6	10.95
f	7.05	18	10.95
g	8	16	8
h	8	15.45	7.45
	8.55	15	7.45

There is no problems as all slacks are +ve.

b) Maximum speed of operation

$$T_{max} = t_{cq} + t_{comb} + t_{su} - t_{cs} = 6 + (0.15 + 0.2 + 0.3 + 0.4) + 4 - 2 = 9.05\text{ ns}$$

$$\text{Or } f = \frac{1000}{9.05} \text{ MHz}$$

c) If the clock skew is  $-7\text{ ns}$

Then the signal at e will arrive at  $7.05\text{ ns}$  the Required time now changes to  
 $T - t_{su} - t_{skew} = 20 - 4 + (-7) = 9\text{ ns}$

There will be no problem as data will arrive at  $7.05\text{ ns}$  and there will be a slack of  $9 - 7.05 = 1.95\text{ ns}$


Q6

a) There are 8 paths in this circuit

- i)  $Q_1 X M Q_4$ , ii)  $Q_2 N X M Q_4$ , iii)  $Q_4 M I_2 Q_1$ , iv)  $Q_5 Q_3$  and finally
- v)  $Q_3 I_1 N X M Q_4$  ← This path clearly is the critical path.

delay of this path in ns:

	$t_{fo}$		
i) FF	$1 * 0.2 + 1 * 0.15$	→	0.35
ii) INV	$2 * 0.1 + 0.08(2.5+1.5) + 0.15$	→	0.67
iii) NAND	$1 * 0.12 + 2 * 0.1 + 0.2$	→	0.52
iv) XOR	$2 * 0.13 + 0.12(1.5+2) + 0.3$	→	0.98
v) MUX	$1 * 0.15 + 2 * 0.14 + 0.4$	→	0.83
			<u>3.35 ns</u>

 

Total delay  $0.7 + 3.35 = 4.05$

Frequency of operation  $= \frac{1}{4.05 + 0.5} = \frac{1000}{4.55}$  MHz

b)

$W = \frac{T_J - T_a}{\theta} \dots T_J = 40 * 1.5 + 70 = 130^\circ C \quad T = 403^\circ K$

$K_T = \frac{T_J}{T_a} = \left(\frac{403}{70+273}\right)^{1.5} \quad K_T = 1.27$

$K_P = (1 + 0.01 * 30) = 1.3$

$K_V = \frac{1}{(1 - 0.01 * 10)} = 1.11$

$K = K_T K_P K_V = 1.27 * 1.3 * 1.11 = 1.83$

Total delay  $= 4.55 * 1.83 = 8.32$  ns

Maximum speed  $\frac{1}{8.32} \approx 120.2$  MHz