

Q1

a)

$-5 + 3$

$5 = 0101$

$3 = 0011$

$-5 = 1010 + 1$

$-5 = 1011$

$$\begin{array}{r} -5 + 3 = \quad 1011 \\ \quad \quad \quad 0011 \\ \hline \quad \quad \quad 1110 \end{array}$$


This a -ve number Convert it to +ve togel its value

Complement and 1

$1110 = 0001 + 0001 = 0010$

This 2 with the -ve sign = -2

b)

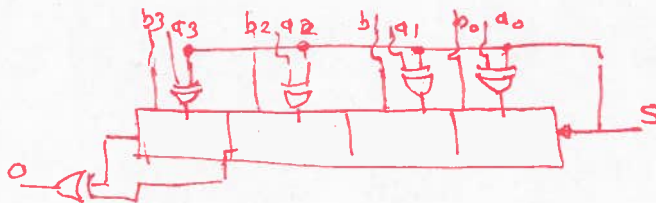

c) $F(x, y, z) = xy + x\bar{z} + yz$ Using Consensus theorem


$= x\bar{z} + yz$

	xy	00	01	11	10
z	0	0	0	1	1
1	0	1	1	0	

$F = \overline{(x+y)(y+\bar{z})} = \overline{(x+y)} + \overline{(y+\bar{z})}$

$F = (x+y)(y+\bar{z})$

By De Morgan's theorem

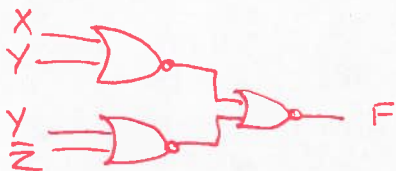



Q2

d)


	W	X	Y	Z	E_0	a	b	c	d	e	f	g
0	0	0	0	0	0	1	1	0	1	0	1	1
1	0	0	0	1	0	1	1	0	0	1	0	1
2	0	0	1	0	0	1	1	0	0	0	0	1
3	0	0	1	1	0	1	1	0	0	0	0	1
4	0	1	0	0	0	1	1	0	1	0	0	1
5	0	1	0	1	0	1	1	0	1	0	0	1
6	0	1	1	0	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	1	0	0	1	0	1
8	1	0	0	0	0	1	1	1	0	0	0	1
9	1	0	0	1	0	1	1	1	0	0	0	1



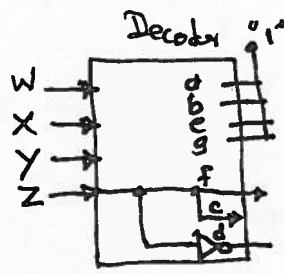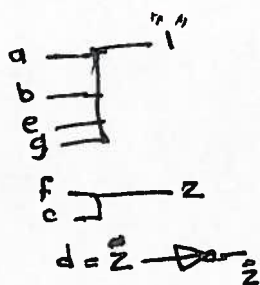$E \rightarrow c, f = 0$ $0 \rightarrow d = 0$
 $a = b = e = g = 1$
 $f = c = Z$ $d = \bar{Z}$



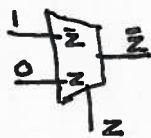b) The decoder has only one inverter to be implemented by a 2-to-1 MUX





Q3
a-b

a)

a	b	D	B
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	0

Half Subtractor

$$\begin{cases} D = a \oplus b \\ B = \bar{a}b \end{cases}$$

$a \rightarrow$  D
 $\bar{a} \rightarrow$  B

m	a	b	B ₋	D	B
0	0	0	0	0	0
1	0	0	0	0	0
2	0	1	0	1	0
3	0	1	0	1	0
4	1	0	0	1	0
5	1	0	0	1	0
6	1	1	1	0	0
7	1	1	1	0	0

ab	00	01	11	10
B ₋ 0	0	2	4	4
1	1	3	7	5

$$D = (\bar{a}b + a\bar{b})\bar{B}_- + (\bar{a}\bar{b} + ab)B_-$$


ab	00	01	11	10
B ₋ 0		1		
1	1	1	1	

$$B = \bar{a}b + B_-(ab + \bar{a}\bar{b})$$

b)

$$\therefore D = a \oplus b \oplus B_-$$

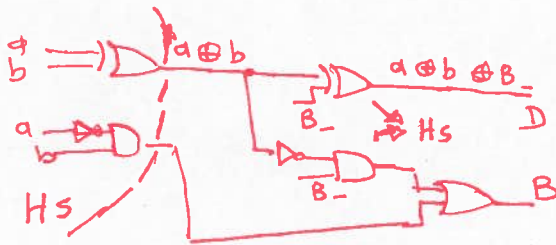
$$B = \bar{a}b + B_-(\bar{a}\bar{b} + ab)$$




2 Half Subtractor & OR gate as shown above make a full subtractor

c)
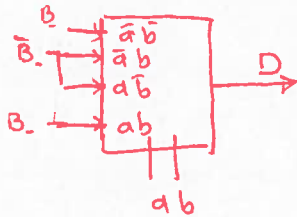
$$D = \bar{a}b\bar{B}_- + a\bar{b}\bar{B}_- + \bar{a}\bar{b}B_- + abB_-$$




$$B = \bar{a}B_- + \bar{a}b + bB_-$$

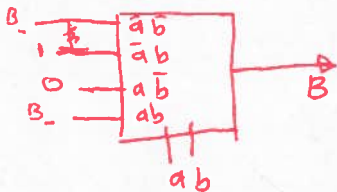

Q4

Results Binary of Addition					Result BCD Addition			
K	A	B	C	D	a	b	c	d
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	0
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	0
5	0	1	0	1	0	1	0	1
6	0	1	1	0	0	1	1	0
7	0	1	1	1	0	1	1	1
8	1	0	0	0	1	0	0	0
9	1	0	0	1	1	0	0	1
10	1	0	1	0	1	0	1	0
11	1	0	1	1	1	0	1	1
12	1	1	0	0	1	1	0	0
13	1	1	0	1	1	1	0	1
14	1	1	1	0	1	1	1	0
15	1	1	1	1	1	1	1	1
16	0	0	0	0	0	0	0	0
17	0	0	0	1	0	0	0	1
18	0	0	1	0	0	0	1	0
19	0	0	1	1	0	0	1	1

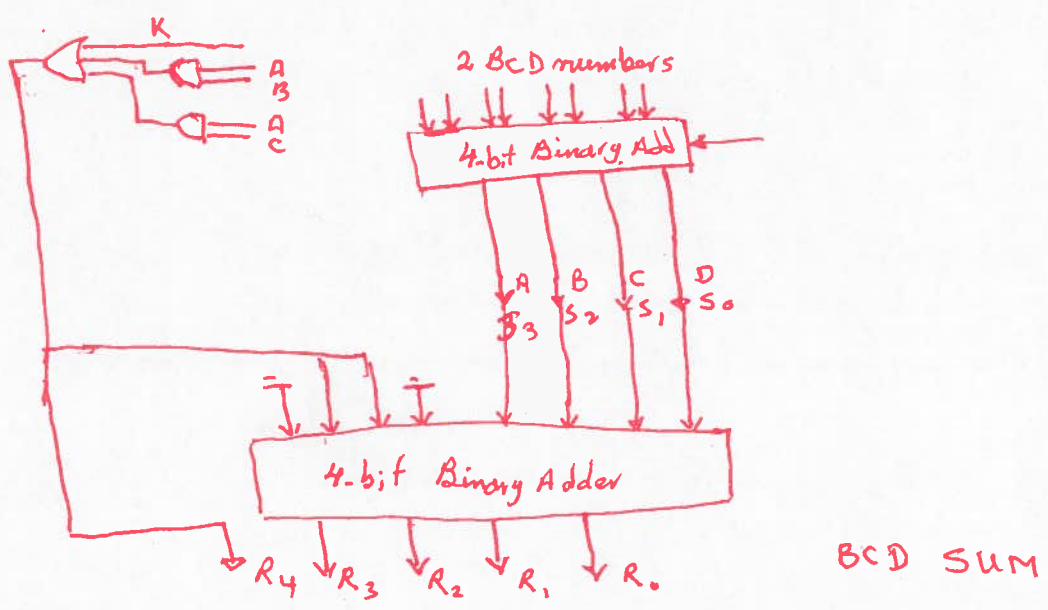
To change the binary to BCD sum we have to add 6 to the group of 9+ as shown in the table above i.e. whenever



BCD SUM

Q5

Y _A Y _B	EF 00	01	11	10
00	00	00	01	11
01	01	01	10	00
11	11	11	00	10
10	10	10	11	01

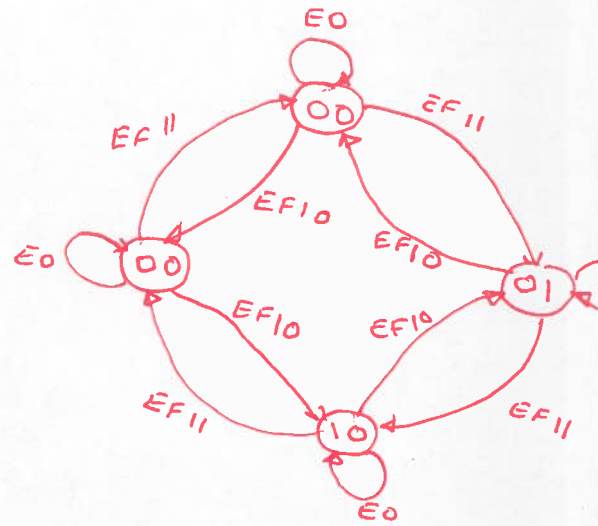

EF	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	1	1	0	1
10	1	1	1	0

Y_A

EF	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1


Y_B

$$Y_A = \bar{E}Y_A + FY_A\bar{B} + \bar{F}Y_A B + E\bar{F}(\bar{Y}_A\bar{Y}_B + Y_A Y_B)$$

$$Y_B = \bar{E}Y_B + E\bar{Y}_A$$

D_A = Y_A = $\bar{E}Y_A + FY_A\bar{B} + \bar{F}Y_A B + E\bar{F}(\bar{Y}_A\bar{Y}_B + Y_A Y_B)$ Eq 1 Excitation for FF A

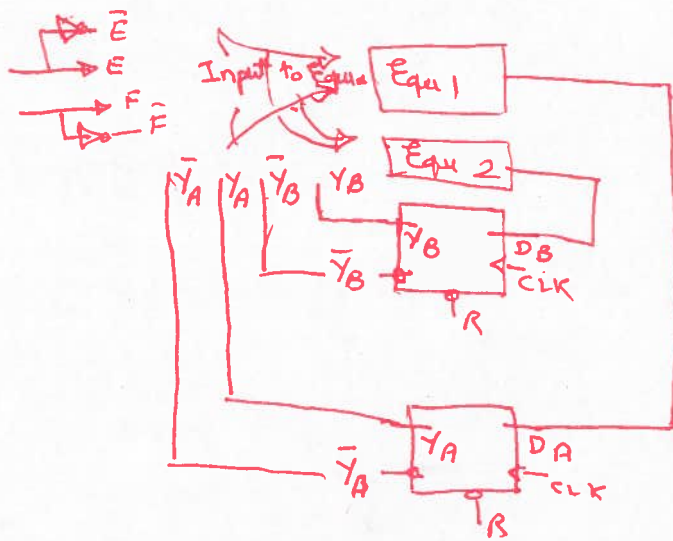D_B = Y_B = $\bar{E}Y_B + E\bar{Y}_A$ Eq 2 Excitation for FF B



Q6

a)

From Diagram


$$T_A = Q_A + Q_B \quad \& \quad T_B = \bar{Q}_A + Q_B$$

Excitation Equations

for T flip flop $Q^+ = T\bar{Q} + \bar{T}Q$

$$\begin{aligned} \therefore Q^+_A &= (Q_A + Q_B)\bar{Q}_A + \overline{Q_A + Q_B}Q_A = \bar{Q}_A Q_B & \text{Equ 1} \\ Q^+_B &= (\bar{Q}_A + Q_B)\bar{Q}_B + \overline{(\bar{Q}_A + Q_B)}Q_B = \bar{Q}_A \bar{Q}_B & \text{Equ 2} \end{aligned} \left. \begin{array}{l} \text{Next State} \\ \text{Equations} \end{array} \right\}$$

Present state		Next State	
Q _A	Q _B	Q _A ⁺	Q _B ⁺
0	0	0	1
0	1	1	0
1	0	0	0
1	1	0	0

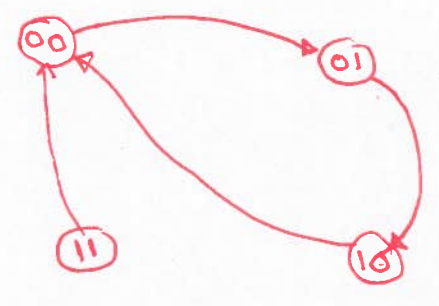

b) The function of this circuit is a counter $00 \rightarrow 01 \rightarrow 10 \rightarrow 00$ with state 11 is not used. The provision in case the counter jumps to 11, then it will go to state 00.