© Zainalabedin Navabi, 1994

PART 7

Synthesis

- **Main concepts**
- **Structural synthesis**
- **Combinational circuits**
- **Functional registers**
- **State machines**

In general:
We will present an overview of synthesis. What is expected from present tools.

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

Hardware Generation

Library Mapping

Optimization

Resource sharing

- Synthesis transforms one hardware format to another
- Results are mapped to a certain library
- Optimization reduces logic
- Resources such as adders can be reused

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

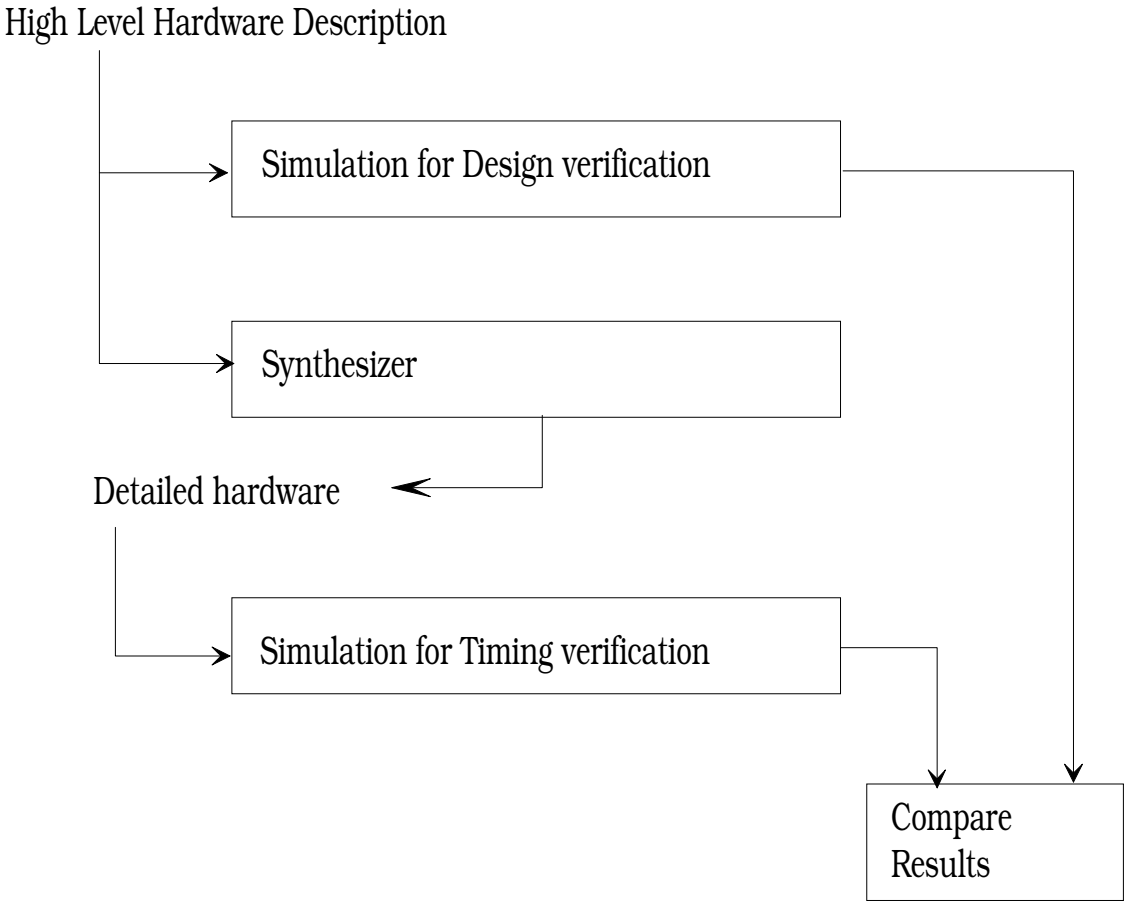

- Design process includes high level simulation
- Synthesizer is used after design verification
- Simulate after synthesis to verify timing

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

Std_logic

Integer

Enumeration types

- Synthesizers support IEEE 1164 mvl9
- Integer type for signals is supported
- Enumeration types are used for states of state machines
- No timing of type TIME is synthesized

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

Can synthesize

Structural

Dataflow

Behavioral

- Can start with *sub_component* specification
- Can use signal assignments
- Can specify functionality in a process statement

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

```
ARCHITECTURE structural OF xnor IS
  COMPONENT xor2 PORT ( i1, i2 : IN BIT; o1 : OUT BIT );
  COMPONENT not1 PORT ( i1 : IN BIT; o1 : OUT BIT );
  SIGNAL x : BIT;
BEGIN
  c1 : xor2 PORT MAP ( i1, i2, x );
  c2 : not1 PORT MAP ( x, o1 );
END structural;
```

- At the structural level, wiring predefined parts are specified
- Parts come from specific technology libraries

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

```
ARCHITECTURE dataflow OF xnor IS
BEGIN
  o1 <= NOT (i1 XOR i2);
END dataflow;
```

- Dataflow specifies bus and register transfers
- Synthesizers generate hardware specified at dataflow level

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.main_concepts

```
ARCHITECTURE behavioral OF xnor IS
BEGIN
  PROCESS ( i1, i2 )
    BEGIN
      IF i1 = i2 THEN
        o1 <= '1';
      ELSE
        o1 <= '0';
      END IF;
    END PROCESS
END behavioral
```

- Behavioral level is the easiest to specify hardware
- Synthesizers use this level for synthesis
- Certain rules must be followed

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.structural_synthesis

```
ARCHITECTURE structural OF counter2 IS
   COMPONENT dff PORT(ck, data : IN BIT; q : OUT BIT);
   END COMPONENT;
   COMPONENT xor2 PORT (i1, i2 : IN BIT; o1 : OUT BIT);
   END COMPONENT;
   COMPONENT not1 PORT (i1 : IN BIT ; o1 : OUT BIT);
   END COMPONENT;
SIGNAL d1, y, d0, y0 : BIT;
BEGIN
   u1 : dff    PORT MAP (clk, d1, y1);
   u2 : dff    PORT MAP (clk, d0, y0);
   u3 : xor2 PORT MAP (y1, y0, d1);
   u4 : not1 PORT MAP (y0, d0);
   count0 <= y0;
   count1 <= y1;
END structural;
```

- Use structural to build larger components form smaller ones
- Can wire full adders into *n_bit* adders
- Hardware is generated from predefined library cells

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.structural_synthesis

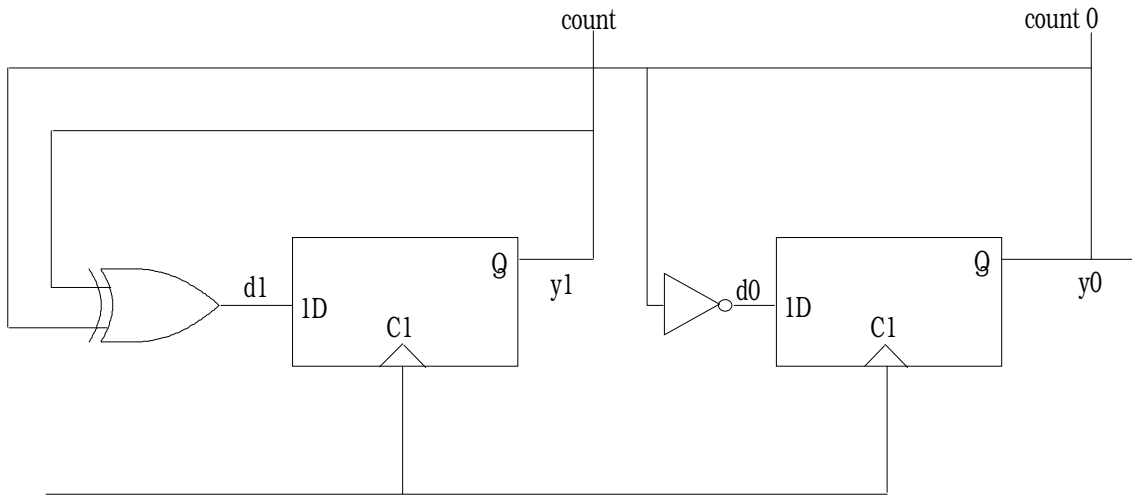

- Hardware generated from structural of counter2
- Can use this design in larger designs
- Can do other parts of design at dataflow or structural
- This way you control parts to use
- Some libraries may include large functional blocks
- Structural synthesis allows use of functional blocks

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.combinational_circuits

```
ENTITY selecting IS
  PORT (a, select_a, b, select_b, c : IN std_logic; z : OUT std_logic);
END selecting;
ARCHITECTURE behavioral OF selecting IS
BEGIN
   PROCESS (a, select_a, b, select_b, c)
   BEGIN
      IF select_a = '1' THEN
         z <= a;
      ELSIF select_b = '1' THEN
         z <= b;
      ELSE
         z <= c;
      END IF;
   END PROCESS;
END behavioral;
```

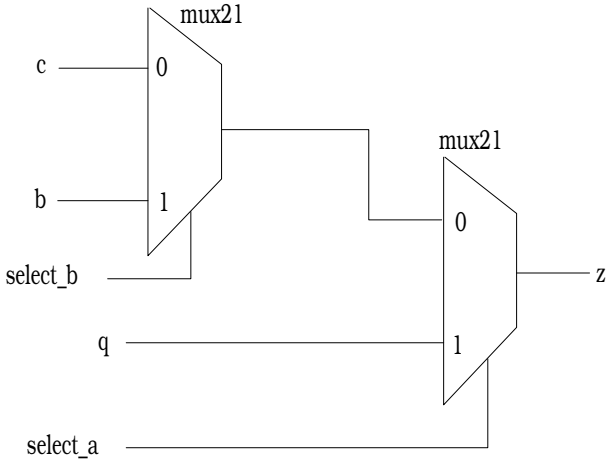

- A behavioral combinational process translates to a combinational circuit
- Process must be sensitive to all inputs
- This process does not store values

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.combinational_circuits

```
ARCHITECTURE dataflow OF selecting IS
BEGIN
        z <= a WHEN select_a = '1' ELSE
                b WHEN select_b = '1' ELSE
                 c;
END dataflow;
```

- Same hardware can be generated by a dataflow description
- In this description AFTER clauses are ignored by the synthesizer
- Can use subprograms for logic functions

© Zainalabedin Navabi, 1994

Synthesis.combinational_circuits

```
.
.
.
bus_a <= reg_1 WHEN put_reg_1_on_bus = '1'
          ELSE "zzzz";
.
.
.
bus_a <= reg_z WHEN put_reg_z_on_bus = '1'
          ELSE "zzzz";
.
.
.
```

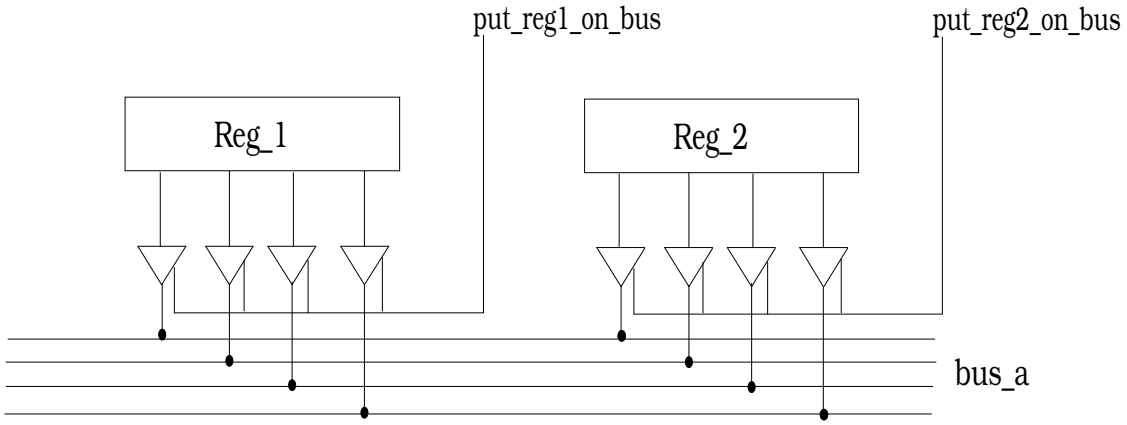

- Bussing can be specified by use of conditional signal assignments
- Assigning "zzzz" is synthesized as opening a *three_state* gate
- Hardware is generated by use of available library cells

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.functional_registers

```
ENTITY counter2 IS
        PORT (clk, reset : IN std_logic;
                count : BUFFER std_logic_vector ( 1 DOWNTO 0));
END counter2;
--
ARCHITECTURE behavioral OF counter2 IS
BEGIN
        PROCESS
        BEGIN
           WAIT UNTIL ( clk'EVENT AND clk = '1' );
           IF  reset = '1' OR count = "11" THEN
                count <= "00";
           ELSE
                count <= count + "01";
           END IF;
        END PROCESS;
END behavioral;
```

- A WAIT in process, implies clocking
- Can also use IF(clk' EVENT AND clk = '1') with sensitivity list
- An edge condition must be the last of IF statement

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.functional_registers

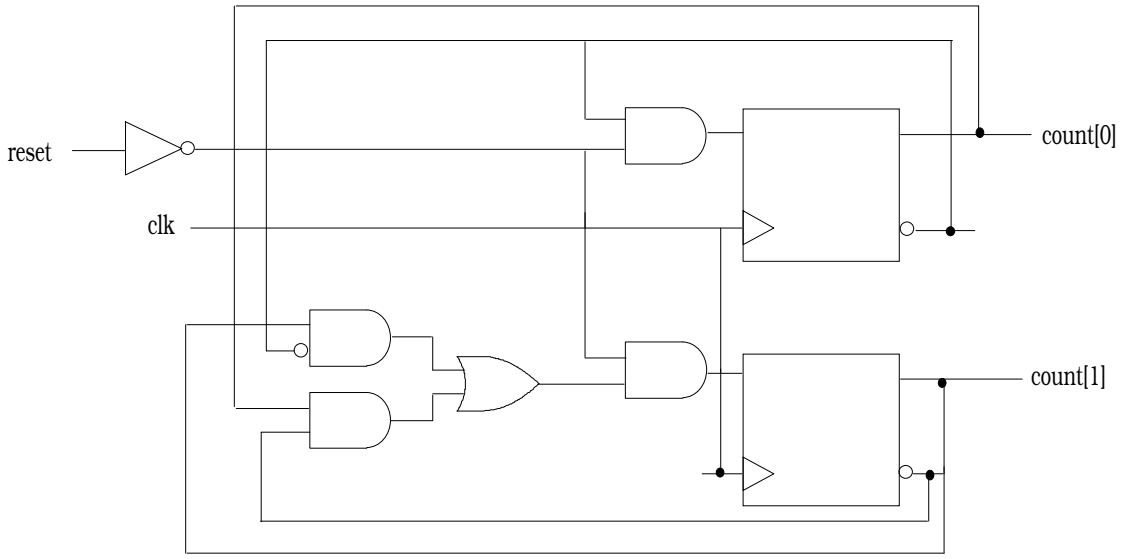

- A possible hardware generated for counter
- Cells from an available library are used

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.functional_registers

```
ARCHITECTURE dataflow OF counter2 IS
BEGIN
   bc : BLOCK ( clk'EVENT AND clk = '1' )
   BEGIN
         count <= GUARDED '00' WHEN reset = '1' ELSE
         count +"01";
   END BLOCK;
END dataflow;
```

- Can also synthesize dataflow descriptions
- A guarded block specifies clocking
- Generates same hardware as behavioral descriptions

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.state_machines

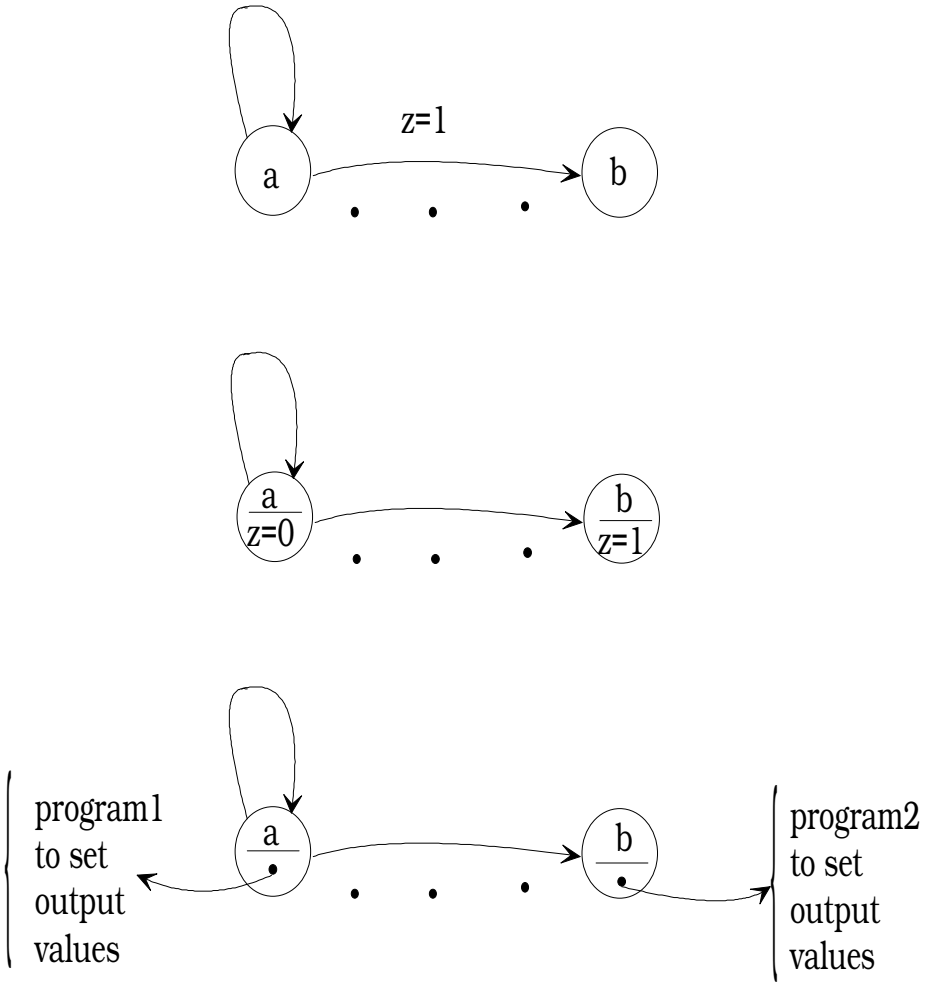

- State machines describe general hardware
- A simple state machine assigns values to outputs
- Synthesizers take state machines with programs with flow instead of simple output values
- Can use high level constructs for such programs

© Zainalabedin Navabi, 1994

Synthesis.state_machines

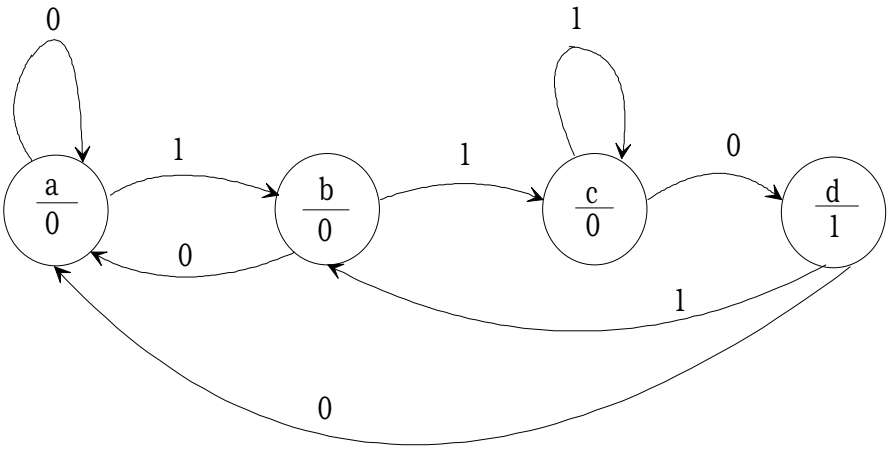

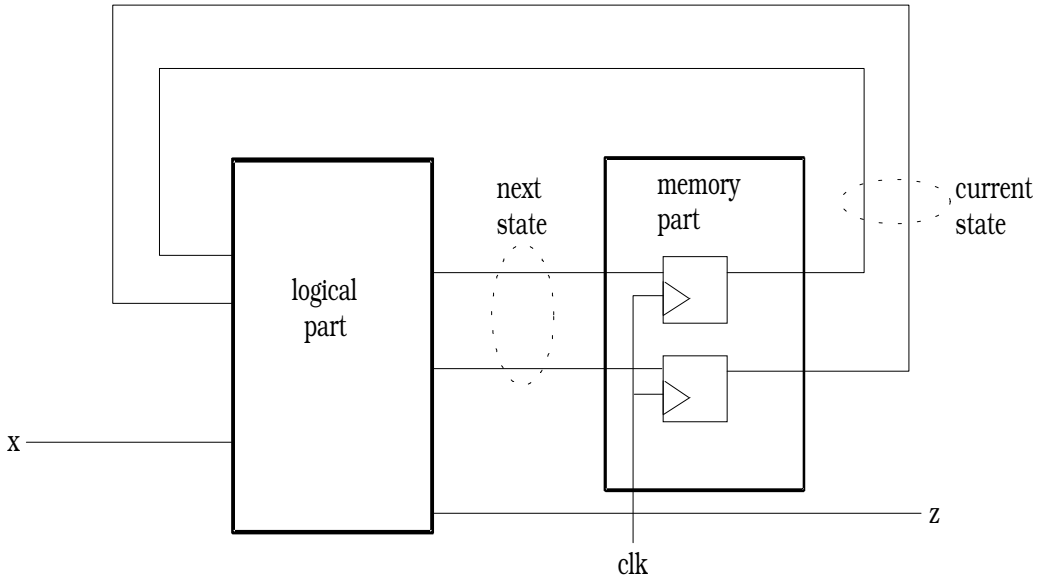

- Can describe state machines with logical and memory parts
- Logical part defines sequencing
- Memory part updates current state with clock

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.state_machines

```
ENTITY detector IS
   PORT ( x, clk : IN std_logic; z : OUT std_logic);
END detector;
---
ARCHITECTURE behavioral OF detector IS
   TYPE state IS ( reset, got1, got11, got110 );
   SIGNAL next_state, current_state : states;
BEGIN
   sequencing : PROCESS ( current_state, x )
   BEGIN
      z <= '0';
      CASE current_state IS
        WHEN reset  =>
           IF x = '0' THEN next_state  <= reset;   ELSE next_state <= got1;
           END IF;
        WHEN got1 =>
           IF x = 0 THEN next_state <= reset;      ELSE next_state <= got11;
           END IF;
        WHEN got11 =>
           IF x = 0 THEN next_state <= got110;   ELSE next_state <= got11;
           END IF;
        WHEN got110;
      z <= '1';
           IF x = 0 THEN next_state <= reset;      ELSE next_state <= got1;
           END IF;
        END CASE;
    END PROCESS;
    clocking : PROCESS ( clk )
    BEGIN
          IF ( clk'EVENT AND clk = '0' ) THEN
             CURRENT_STATE <= NEXT_STATE;
    END IF;
    END PROCESS;
END behavioral;
```

- Sequencing PROCESS for logical part
- Clocking PROCESS for memory part

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.state_machines

Hardware design

1.	Design state machine use programs between states use CASE, IF_THEN, ... for assigning output values

2.	Partition into data and control synthesize data units synthesize control unit by a state machine

- Two design methods both use state machine descriptions
- Next two parts will present these methods

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

Synthesis.conclusions

1. Outline: Introduction, Organization, Outline

2. Review: Levels of abstraction, Entity and Architecture, Signal assignments, Guarded signal assignments, Three state bussing, Process statements, Combinational processes, Sequential processes, Multiplexing, Package

3. MSI Based Design: Use MSI parts of Part 2, Sequential multiplication, Designing the multiplier, Control and data parts, Testing the multiplier

4. General CPU Description: Will present a high level VHDL description of a small CPU. The CPU, Memory organization, Instructions, Addressing, Utilities for VHDL description, Interface, Behavioral description, Coding individual instructions

5. Manual Data_path Design: Will present VHDL description for manual design of data_path. Data components, Bussing structure, Description of logic, Description of registers, Bus resolutions, Component wiring

6. Manual Controller Design: Will present VHDL description for manual design of controller. Controller hardware, VHDL style, Signals and resolutions, State descriptions, Complete CPU, Testing CPU

7. Synthesis: Main concepts, Structural synthesis, Combinational circuits, Functional registers, State machines

8. Behavioral_Synthesis: Will present a high level synthesizable CPU description. Synthesis style, Necessary Package, Interface, General Layout, Registers, Clocking, Sequencing, Simulation and Synthesis

9. Dataflow_Synthesis: Will partition the CPU and synthesize each part separately. Synthesis style, Controller, Data components, Data path, Synthesized example, Conclusions

© Zainalabedin Navabi, 1994